

LAB 5 - RTD Lab PREP

3.35 ①

RTD

- We will be using a simulator box with ~~RTD simulator~~ with a slide switch
- It changes resistance as you change the switch.


INSTR

~~INSTR~~

- The amp used to measure the voltage difference across the bridge.

Procedure

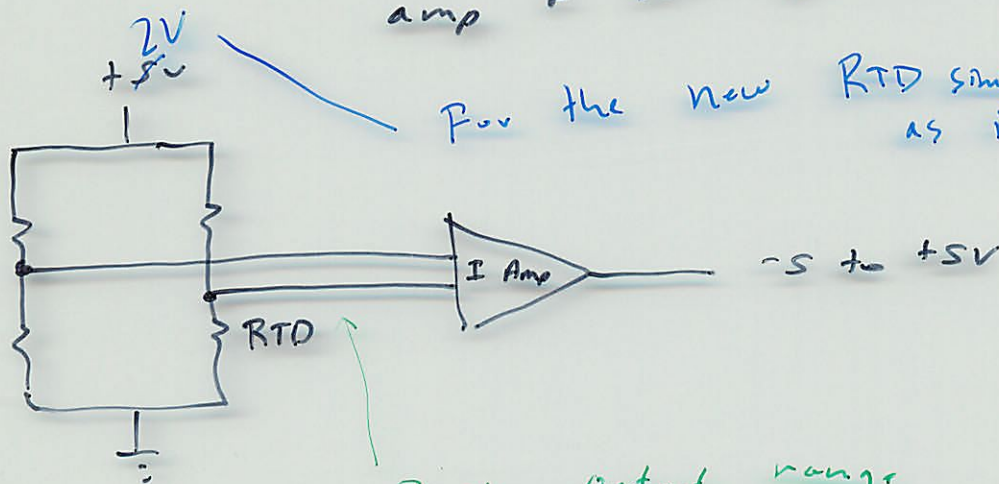- Calculate RTD $R @ 0^\circ + 100^\circ C$
- Place them in a bridge & calculate bridge output for those inputs.
- Place these numbers into an instrumentation amp & set up for $\pm 5V$.



Bridge output range

$$0^\circ C = 0V$$


$$100^\circ C = 404mV$$

$$\therefore \text{Gain} = \frac{\Delta I_{A \text{ out}}}{\Delta \text{Bridge out}} = \frac{\Delta V_{out}}{\Delta V_{in}}$$

New RTD Simulator 2008


52

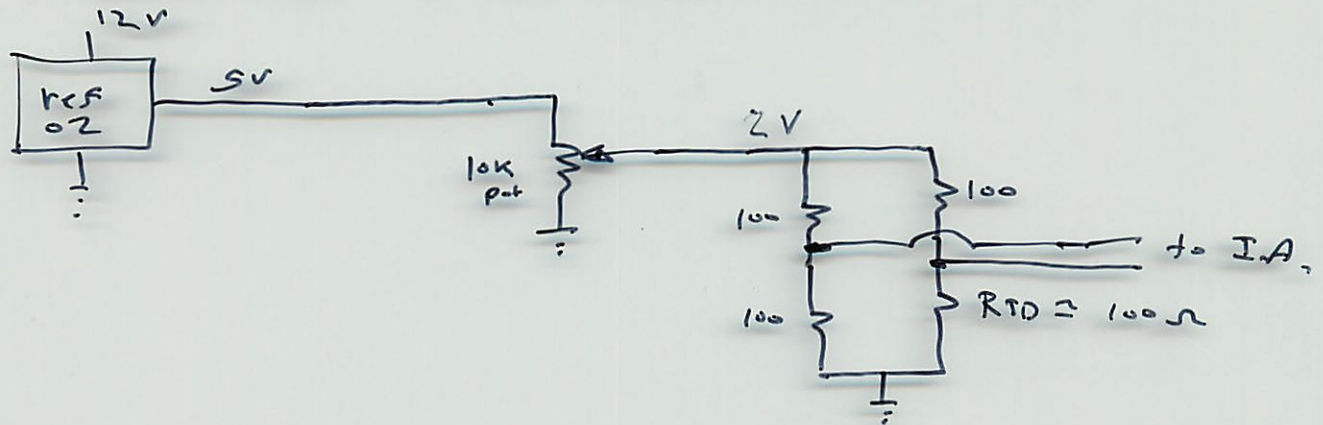- Need to feed 2V into bridge rather than 5V (too much current to sink)



- make sure you turn the RTD Simulator off to save the 9V ~~batt~~ battery life.

4wires → use 2 module wires

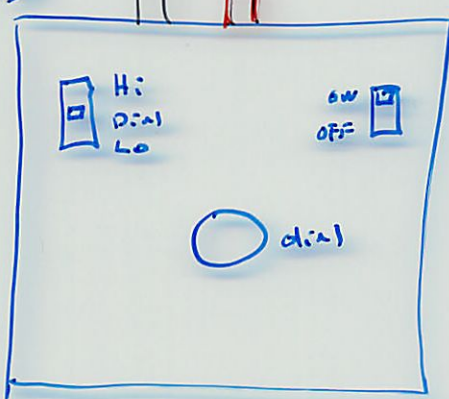

- we set $L_0 = 0^\circ\text{C}$
 $H_i = 100^\circ\text{C}$


- default is a Platinum RTD with $\alpha = 0.00385$

- fine dial just rotate
- coarse dial - push & rotate.

Demo: 1) Set to L_0 & measure 100Ω on DMM
2) Set to H_i & measure R_T on DMM

$$\begin{aligned}
 R_T &= R_0 (1 + \alpha T) \\
 &= 100\Omega (1 + 0.00385 \cdot (100 - 0)) \\
 &= 100 (1.385) = \boxed{138.5\Omega}
 \end{aligned}$$

Lab 5 - Circuit

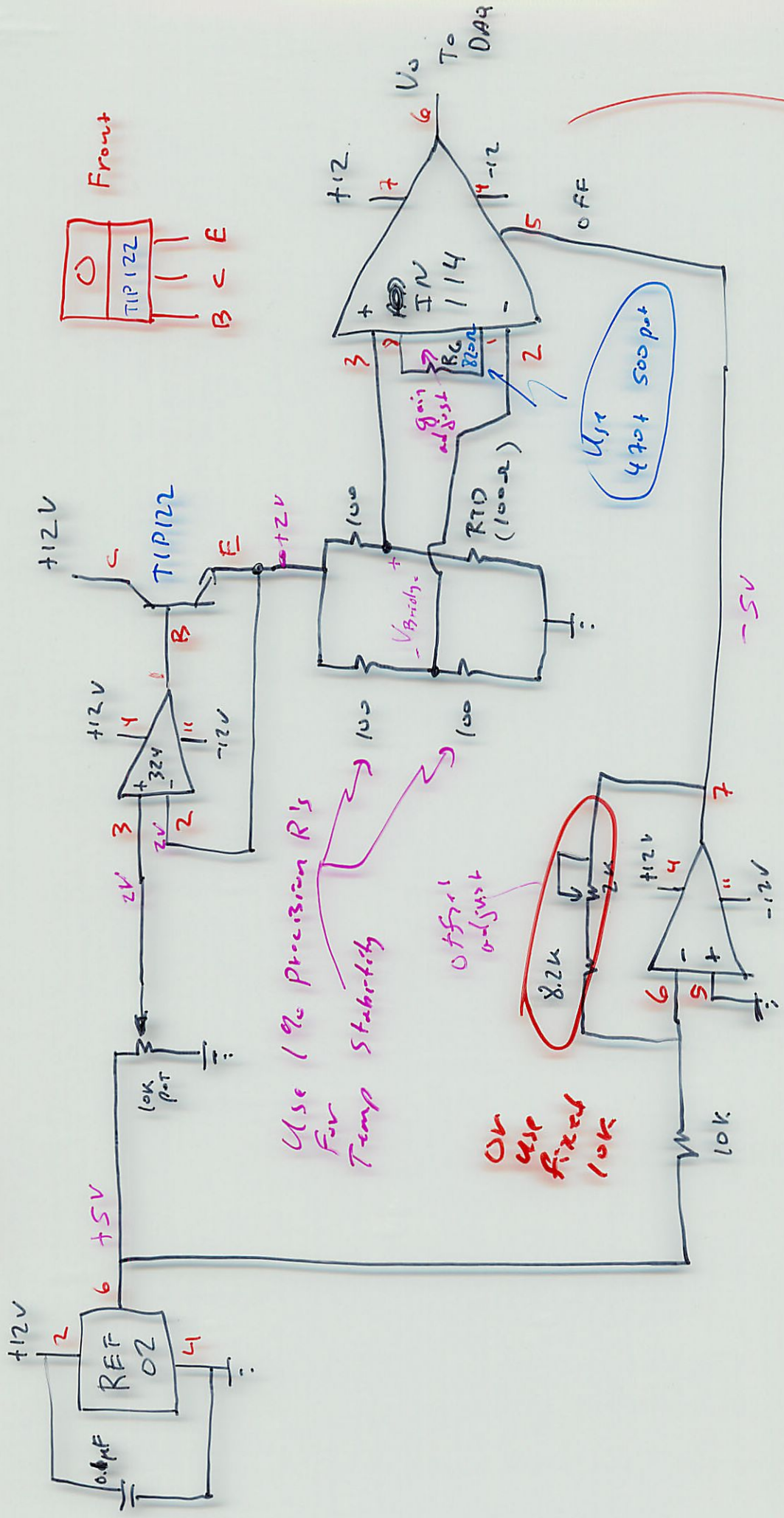

Front
TIP122
B C E

$$G = 1 + \frac{50k}{R_G}$$

$$R_G = 820\Omega$$

$$A_{Vr} = -1$$

$$V_{BRIDGE} = V_S \left(\frac{R_{TD}}{R_T + R_{TD}} \right) - V_S \left(\frac{R}{R+R} \right)$$

2V

$$R_{TD} = R_o + R_{oAT}$$

when $\alpha = 0.99385$

$$V_{DAQ} = A \cdot V_{BRIDGE} + V_{OFF}$$

Pre lab

(4)

4a) $R_T = R_0 (1 + \alpha T)$

$$R_0 = 100 = R_c$$

$$\alpha = 0.00385$$

$$R_T = 100 (1 + 0.00385 T)$$

for $T = 0^\circ\text{C}$

$$R_T = 100$$

for $T = 100^\circ\text{C}$

$$R_T = 138.5$$

inverse transfer fnc for lab is

$$T = \frac{R_T - 100}{0.385}$$

4b) $V_B = V_S \cdot \frac{R_T}{R_c + R_T} - \frac{V_S}{2}$

$$V_S = 2V$$

$$100 \text{ to } 138.5 \Omega$$

$$= 2 \cdot \frac{R_T}{R_c + R_T} - 1 = \frac{2 R_T}{100 + R_T} - 1$$

inverse transfer fnc for lab is

$$R_{TDr} = R_T = \frac{2 + 2V_B}{(2 - 2V_B)} \times 100 \quad R_c$$

4c) $R_G = \frac{50K}{A-1}$

$$A = 62$$



$$R_G = \frac{50K}{62-1} = 820 \Omega$$

$$V_O = 62 V_B - 5V$$

inverse transfer fnc for lab is:

$$V_B = \frac{(V_O + 5)}{62}$$

Lab 5 2012 Handout

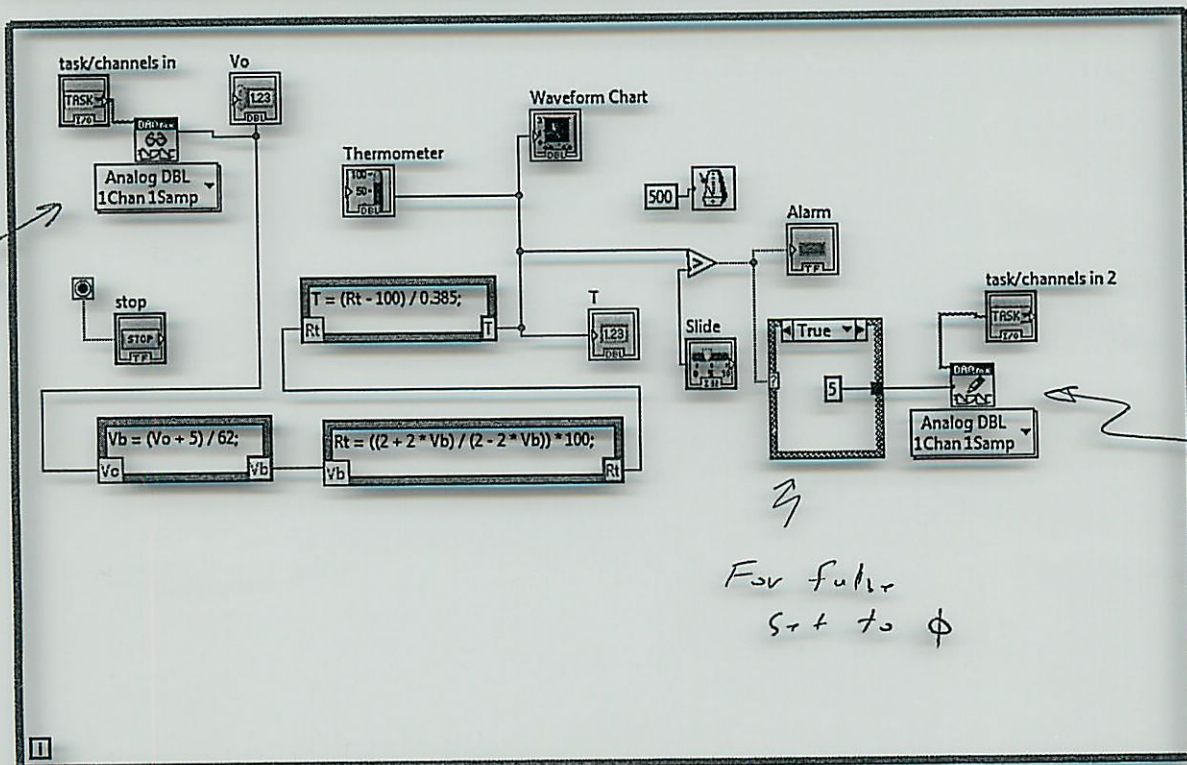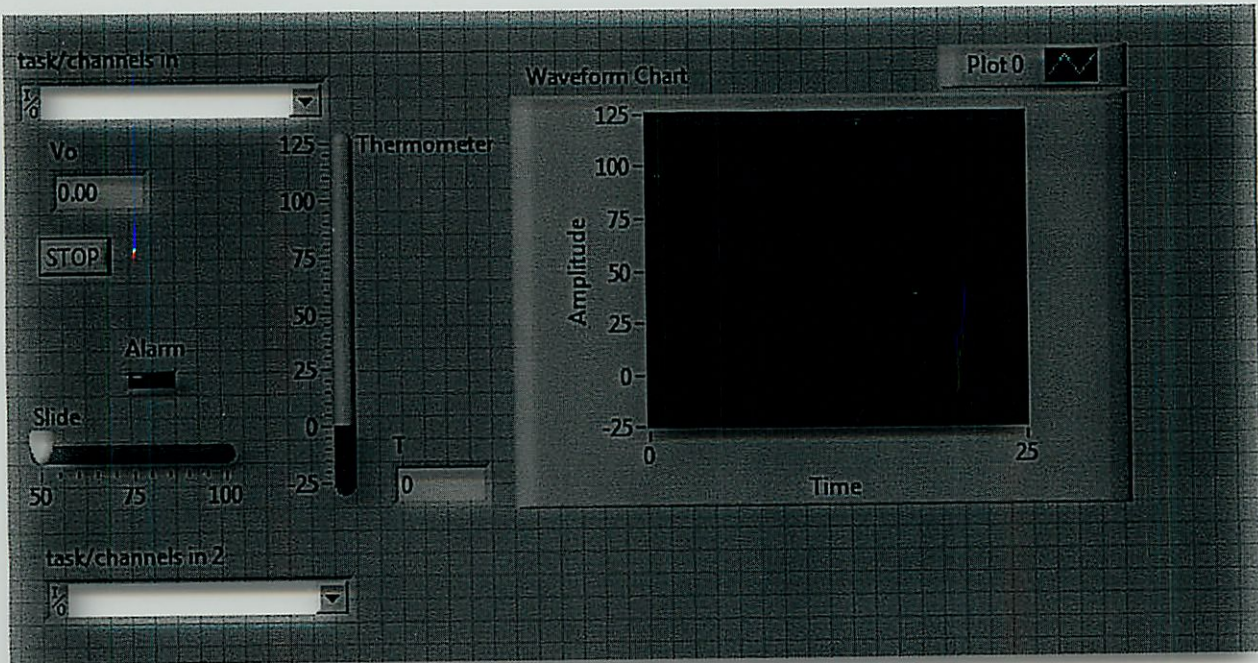

Green Wire

Blue Wire

For future set to ϕ